


Electric Circuits

power $P = \frac{\text{energy}}{\text{time}} = \text{rate of energy conversion}$

$$[\rho] = J_S = \text{watt (W)}$$

Inside current-carrying resistor, electrostatic potential energy is converted into thermal energy (heat) at a rate:

$$P = I V$$

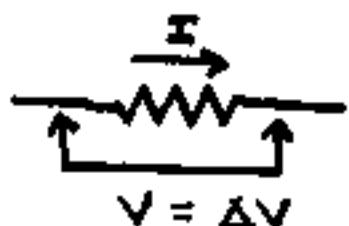

inside resistor:

$$\textcircled{1} \quad \nabla V = \text{const}$$

$$\Delta \text{PE} = \Delta U = q \Delta V \quad (\text{PEV})$$

Where did PE go? Not into KE.

$\text{KE} = \text{const}$, since drift velocity $v_d = \text{const}$.

PE converted into heat

$$\Delta N \text{ q's pass in time } \Delta t \Rightarrow I = \frac{\Delta Q}{\Delta t} = \frac{\Delta N}{\Delta t} q$$



$$P = \frac{\Delta U}{\Delta t} = \frac{\Delta N \cdot g \Delta V}{\Delta t} = I \cdot \Delta V \quad \checkmark$$

"100 W" lightbulb \rightarrow 100 J_s converted to heat/light

For all household appliances: $\Delta V = 120V$ 95% 5%



$$P = \frac{V^2}{R} \Rightarrow \text{IF } V = \text{const} = 120V, \text{ then}$$

ρ big \Leftrightarrow R small

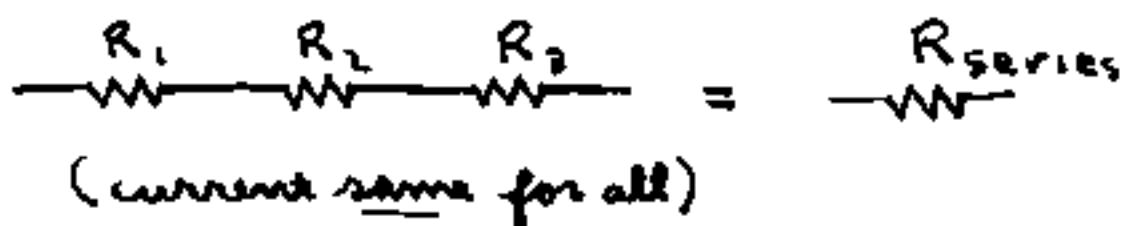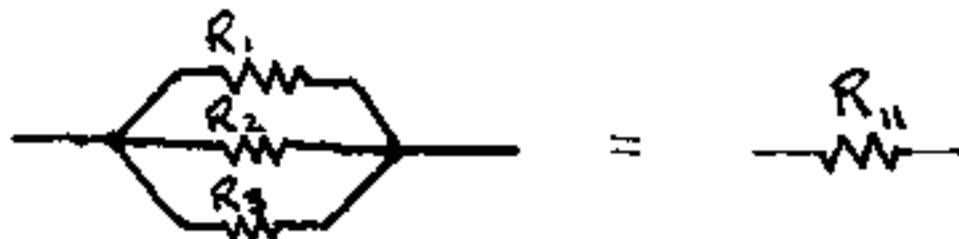Combinations of resistorsin seriesin parallel(ΔV same for all)

$$R_{\text{series}} = R_1 + R_2 + R_3$$



$$\frac{1}{R_{\text{parallel}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \Leftrightarrow R_{\text{parallel}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

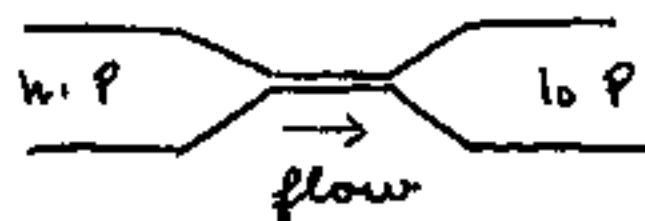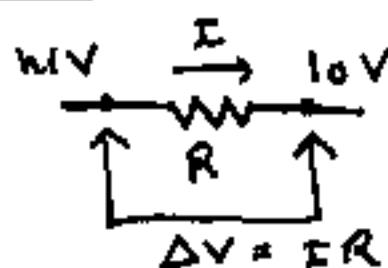Adding R in series always increases R_{total}.Adding R in parallel always decreases R_{tot}.Charge/water analogy

Think of voltage as "electrical pressure"
 (+) charges want to flow from hi V to lo V,
 just as water in a pipe wants to flow from
 hi P to lo P.

A battery acts like a "charge pump",

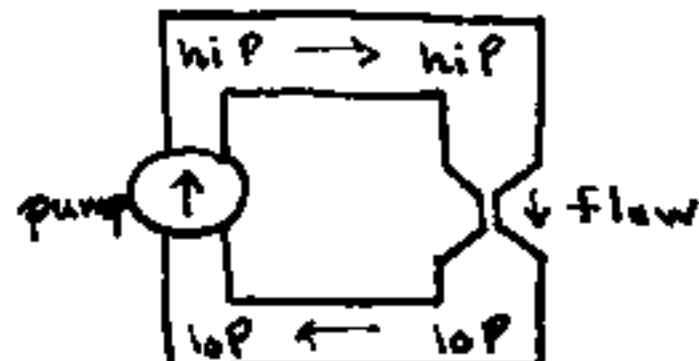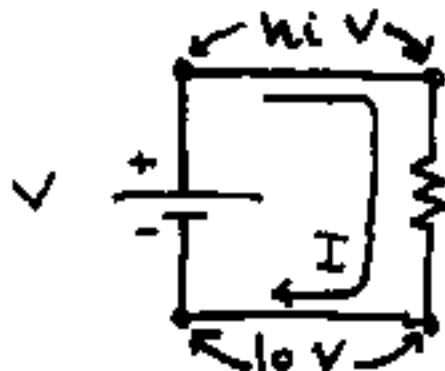Battery pumps (+) charges "uphill" in the direction they don't want to go, from (-) terminal to (+) terminal.



- inside resistor, (+) charges flow "downhill" $hiV \rightarrow loV$
- inside battery, (+) charges are pumped "uphill" $loV \rightarrow hiV$


To analyze circuits need Kirchhoff's 2 Laws

* K1 : Loop Law (Voltage Law)

For any closed loop in a circuit,

sum of voltage rises = sum of voltage drops

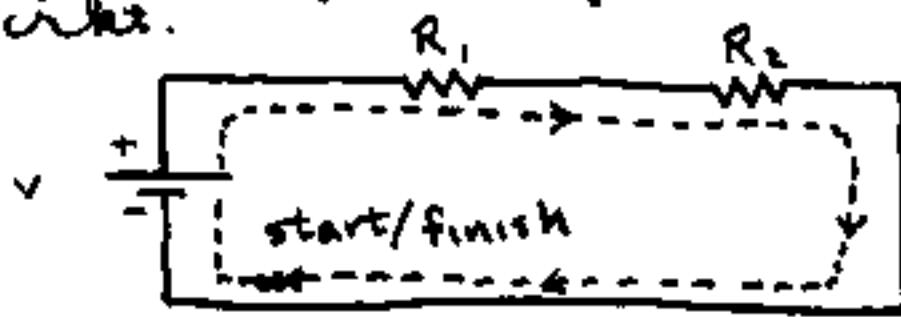~ must be so, since must return to same voltage after complete loop returning to original spot in circuit.



Chose to go around loop in same dir. as current.


$$\underbrace{V}_{\text{rise}} = \underbrace{IR_1}_{\text{drop}} + \underbrace{IR_2}_{\text{drop}} = I(R_1 + R_2)$$

$$I = \frac{V}{R_1 + R_2}, \quad \text{Voltage across } R_2 = V_2 \\ = V_2 = IR_2 = V \cdot \left(\frac{R_2}{R_1 + R_2} \right)$$


"voltage divider"

• K2 Junction Law (Current Law)

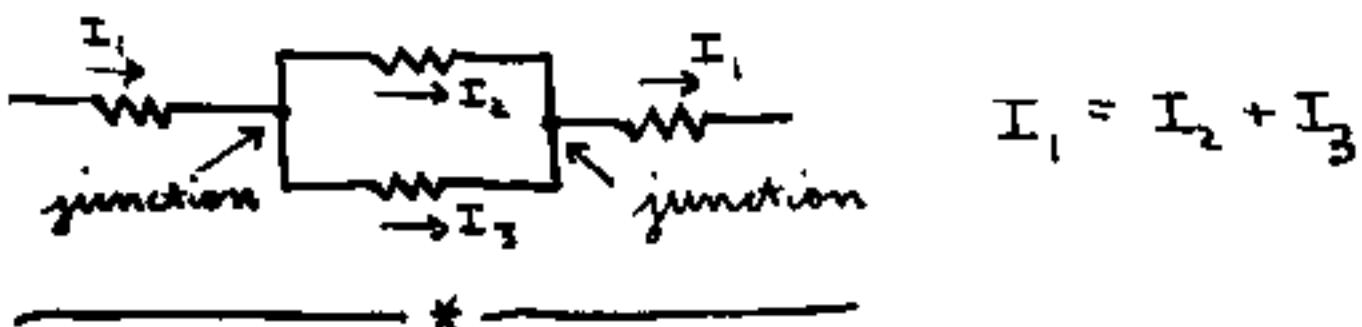For any junction (place where 3 or more wires meet), total current in = tot current out.



Creates w/ multiple loops and batteries

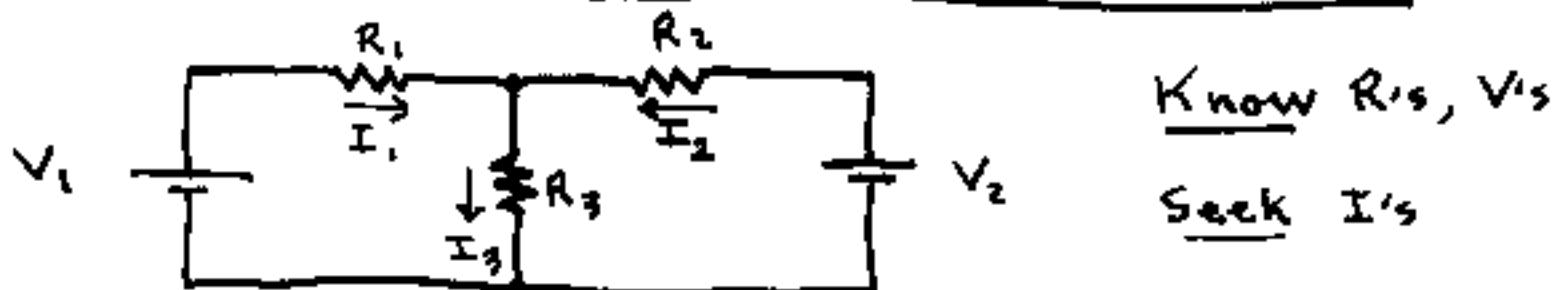

3-step procedure:

I. Guess direction of I thru each R.


Draw I arrows, label each. Direction of I not always obvious, so just guess. If guess is wrong, current I will come out w/ negative value after numbers are plugged in

II. Junction Law (K2) gives 1 or more eq'mns

$$\text{Eq'n (1)} \quad I_1 + I_2 = I_3$$

(3 unknowns: $I_1, I_2, I_3 \Rightarrow$ need 3 eq'n's)

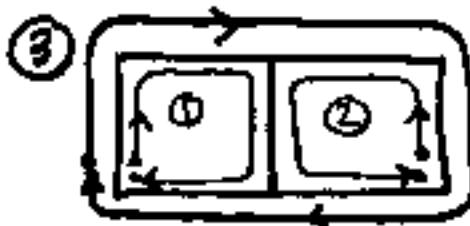III. Loop Law (Voltage Law) gives eq'n for each loop



Only need 2 more eq'n's
(in this example) \Rightarrow
only 2 of 3 loops needed.

$$\text{Loop } ① \quad +V_1 - I_1 R_1 - I_3 R_3 = 0 \quad (\text{Eq'n 2})$$

$\underbrace{+V_1}_{\text{rise}} \quad \underbrace{- I_1 R_1}_{\text{drop}} \quad \underbrace{- I_3 R_3}_{\text{drop}}$

$$\text{Loop } ② \quad +V_2 - I_2 R_2 - I_3 R_3 = 0 \quad (\text{Eq'n 3})$$

Loop ③ (Don't need because already have 3 eq'n's)

$$+V_1 - I_1 R_1 + I_2 R_2 - V_2 = 0$$

$\underbrace{+V_1}_{\text{rise}} \quad \underbrace{- I_1 R_1}_{\text{drop}} \quad \underbrace{+ I_2 R_2}_{\text{rise!}} \quad \underbrace{- V_2}_{\text{drop!}}$

Remember:

if traveling "upstream"
(against I), then
 V rises, ΔV is $(+)$

if traveling from $(+)$ to $(-)$ terminal,
 V drops, ΔV is $(-)$

3 eq'n's in 3 unknowns:

$$(1) \quad I_3 = I_1 + I_2$$

$$(2) \quad V_1 = I_1 R_1 + I_3 R_3$$

$$(3) \quad V_2 = I_2 R_2 + I_3 R_3$$

$I_1 = (I_3 - I_2)$ plug into (2) \Rightarrow 2 eq'n's in 2 unk's: I_2, I_3

Circuit probes:


Ammeter measures current thru itself




Voltmeter measures voltage diff between its terminals



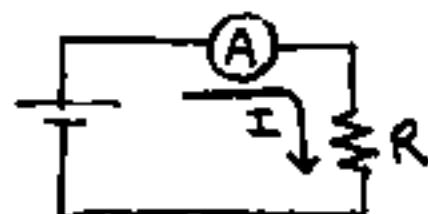To measure current thru R , must place ammeter in series




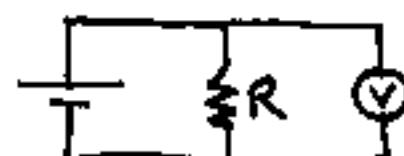To measure voltage across R , must place voltmeter in parallel




Ideal ammeter has $r_{internal} = 0$ so measured

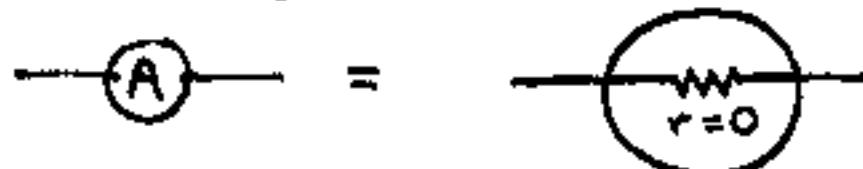current is not affected by presence of ammeter:



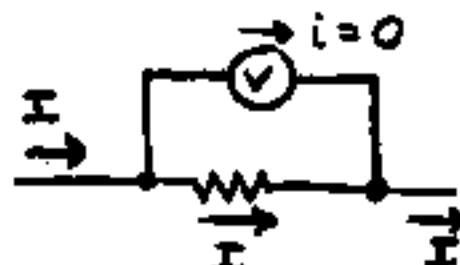Ideal voltmeter has $r_{internal} = \infty$, so no I flows thru voltmeter \Rightarrow currents, voltages in rest of circuit are not affected



RC Circuits

Simplest RC circuit: capacitor C , charged to voltage $V_0 = \frac{Q_0}{C}$, attached to resistor R , w/ switch.



$$C = \frac{Q}{V} \Rightarrow V_0 = \frac{Q_0}{C}$$

\downarrow
"initial"

Close switch at $t = 0$, current I starts to flow.



$$\text{At } t = 0^+, I_0 = \frac{V_0}{R}$$

$$I = -\frac{dQ}{dt} \quad (-\text{sign since } Q \text{ is decreasing})$$

$$V_{\text{across } C} = V_{\text{across } R}, \quad V_C = V_R, \quad \frac{Q}{C} = IR,$$

$$\frac{Q}{C} = -\frac{dQ}{dt} \cdot R,$$

$$\boxed{\frac{dQ}{dt} = -\frac{1}{RC} \cdot Q} \quad *$$

RC = "time constant" τ , has units of time

$$[R][C] = \frac{A}{X} \cdot \frac{\text{coulombs}}{X} = \frac{\text{coul}}{\text{coul/s}} = \text{s (seconds)}$$

* is a differential eq'n of the form: $\frac{dx}{dt} = \underbrace{a \cdot x}_{\text{const}}$

rate of change of $x \propto x \Leftrightarrow$ exponential sol'n


$$x = x_0 e^{at} \quad \text{Check: } \frac{dx}{dt} = a \cdot x_0 e^{at} = a \cdot x \checkmark$$

$a > 0 \Rightarrow$ exponential growth

$a < 0 \Rightarrow$ exponential decay

$$Q(t) = Q_0 e^{-t/\tau_{RC}}$$

$$= CV_0 e^{-t/\tau}$$

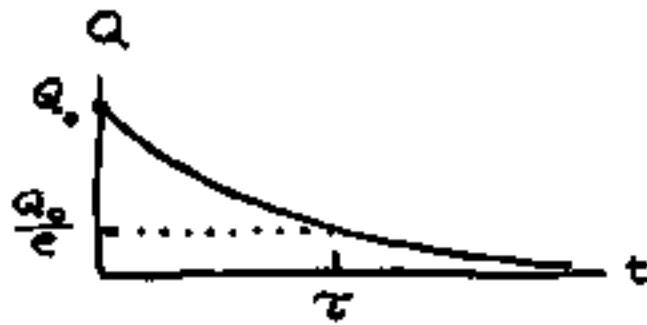


In time τ , Q falls by factor of $1/e \approx 0.37$

In time 2τ , Q falls by factor of $(1/e)(1/e) \approx 0.14$
etc.


$\Rightarrow Q$ approaches zero asymptotically, so does V, I

$$V = \frac{Q}{C}$$

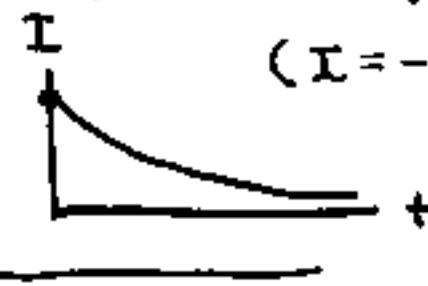

$$(I = -\frac{dQ}{dt} = +\frac{V_0}{R} e^{-t/\tau})$$

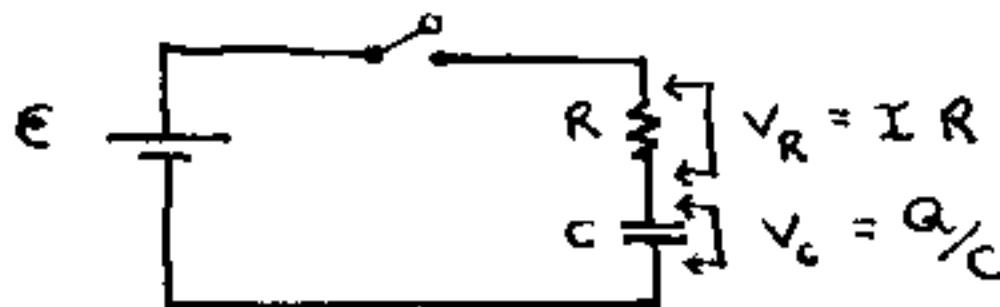More complex RC circuit: Charging C w/ battery



Before switch closed, $I=0, Q=0$

Close switch at $t=0$. Now $\epsilon = V_R + V_C$


Charge Q and voltage $V_C = Q/C$ of capacitor cannot change instantly (takes time for Q to build up).

At $t=0+$, $Q=0$, $V_C=0$, $\epsilon = V_R = IR \Rightarrow I_0 = \epsilon/R$


(Although Q on capacitor cannot change instantly, current $I = dQ/dt$ can.)

"Current thru a capacitor"

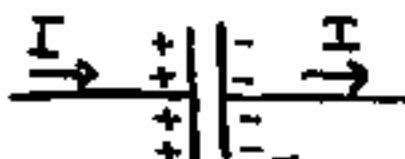~ even though no charge passes between plates.



$+Q/-Q$ increasing as I flows

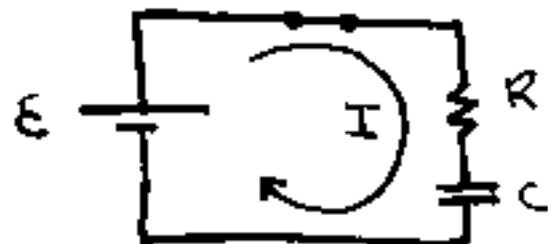

$$\epsilon = V_R + V_C$$


$$\epsilon = IR + Q/C$$

$$\epsilon = + \frac{dQ}{dt} \cdot R + Q/C$$

As $t \rightarrow \infty$, $Q \rightarrow \infty$, $V_C = \frac{Q}{C} \rightarrow \infty$, $V_R \downarrow$, $I = \frac{V_R}{R} \downarrow$

After long time, $t \gg \tau = RC$, $I = 0$, $V_C = \epsilon$, $Q = C \cdot \epsilon$

$$V_C = \frac{Q}{C}$$

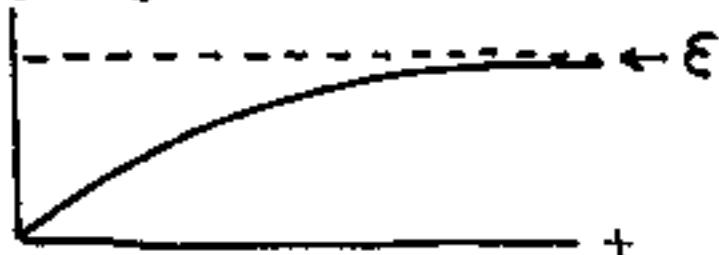


$$V_C(t) = \epsilon (1 - e^{-t/RC})$$

Things to remember:

- Uncharged capacitor acts like a "short": $V_C = \frac{Q}{C} = 0$
- After long time, when capacitor is fully charged, it acts like "open-circuit". Must have $I_C = 0$ eventually, otherwise $Q \rightarrow \infty$.


House Wiring

Wall socket
= 3-prong plug

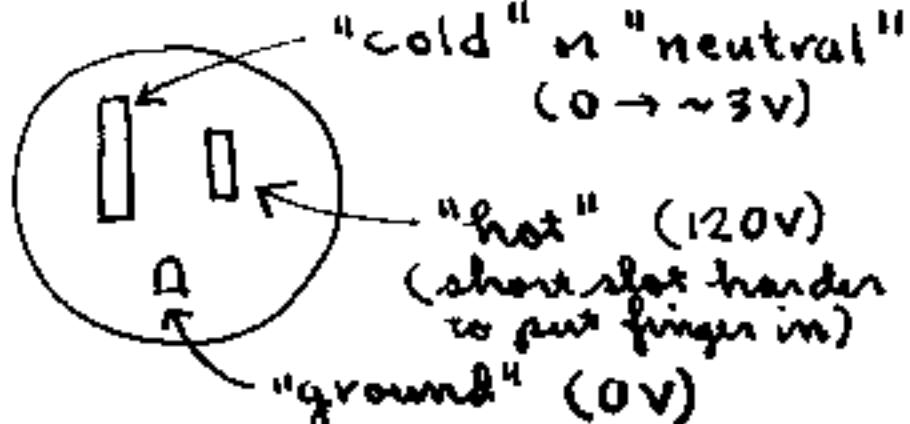


"hot" voltage is AC, not DC

Battery voltage is DC = const in time

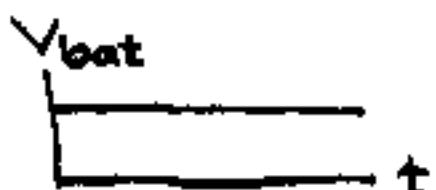

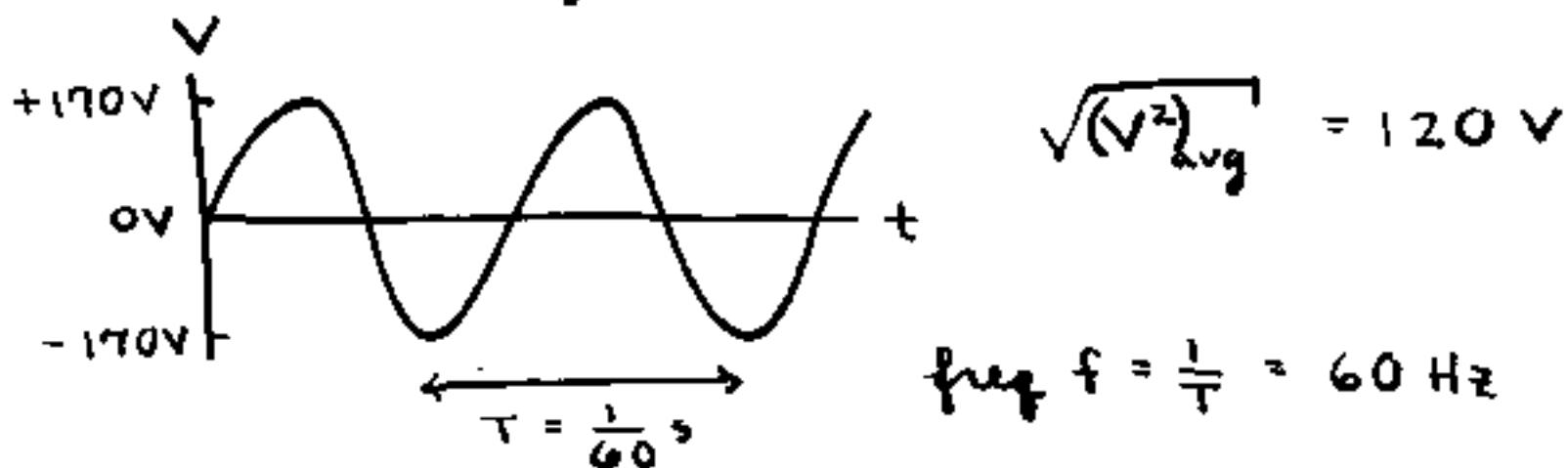
Wall socket voltage is AC = sinusoidal in time



AC voltage is more economical to distribute from power plant to homes than DC.

Standard electrical wiring colors:

black = hot (burnt black)	}	Never assume house wiring is correct - always test !
white = cold (like snow)		
green = ground (grass)		

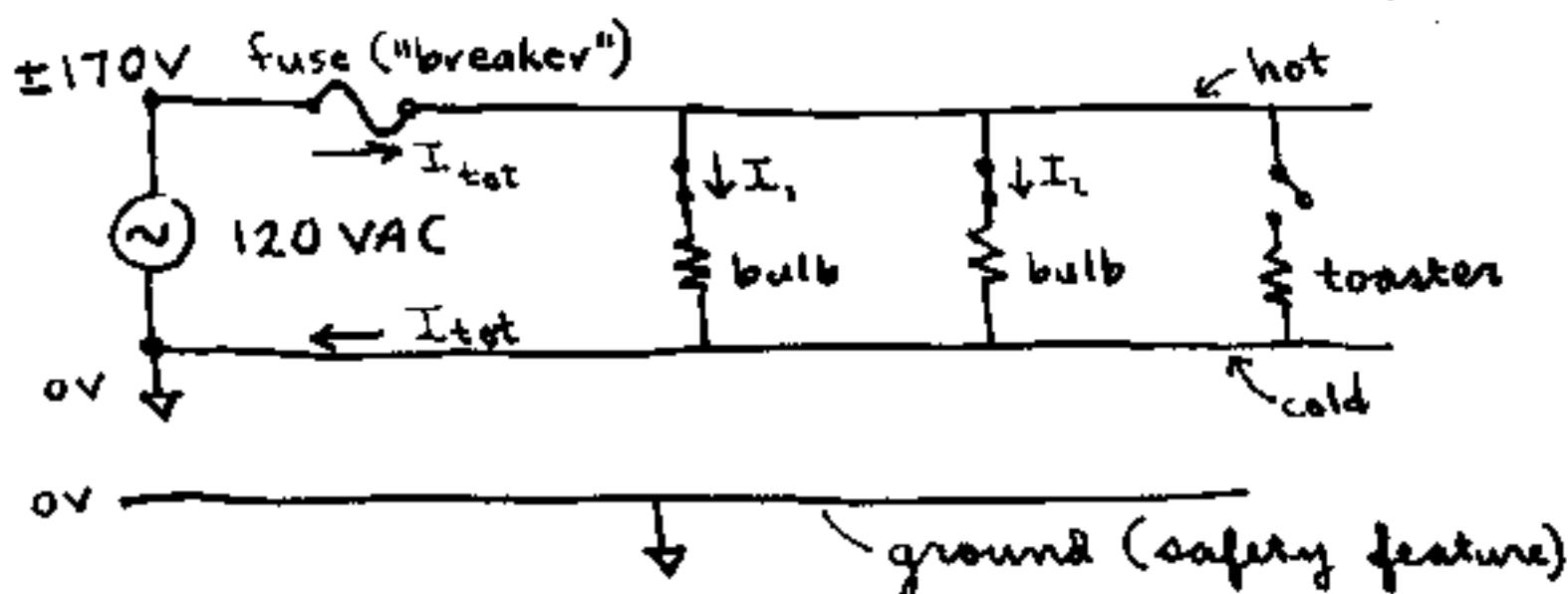

If $I_{tot} > 15A$, breaker opens, preventing wires from over-heating

Chassis case of appliances are connected to ground as safety precaution.