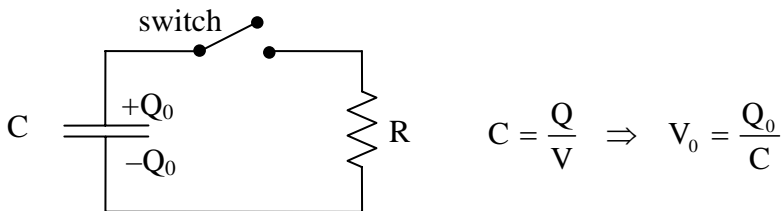



## RC Circuits

An RC circuit is a circuit with a resistor (R) and a capacitor (C). RC circuits are used to construct timers and filters.

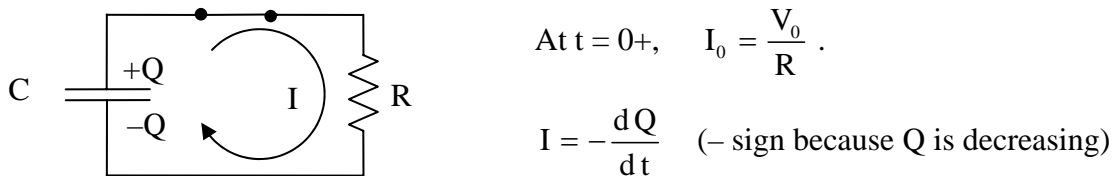**Example 1. Very simple RC circuit:** a capacitor C, charged to an initial voltage  $V_0 = Q_0/C$ , attached to a resistor R with a switch.



Close the switch at time  $t = 0$ , so current  $I$  starts to flow. The charged capacitor is acting like a battery: it produces a voltage difference across the resistor which drives the current through the resistor:



$$V_{\text{across } C} = V_{\text{across } R}, \quad V_C = V_R, \quad \frac{Q}{C} = IR, \quad \frac{Q}{C} = -\frac{dQ}{dt} \cdot R, \quad \boxed{\frac{dQ}{dt} = -\frac{1}{RC} Q} \star$$

$RC = \text{"time constant"} = \tau$ , has units of time

$\star$  is a differential equation of the form  $\frac{dx}{dt} = a \cdot x$ , where  $a$  is a constant.

This equation says: (rate of change of  $x$ )  $\propto x \Leftrightarrow$  exponential solution:  $x = x_0 \exp(at)$

$$\text{Check: } \frac{dx}{dt} = \frac{d(x_0 \cdot e^{at})}{dt} = a \cdot x_0 \cdot e^{at} = a \cdot x . \quad \text{It works!}$$

$a > 0 \Rightarrow$  exponential growth,  $a < 0 \Rightarrow$  exponential decay


$$\text{The solution to } \frac{dQ}{dt} = -\frac{1}{RC} Q \quad \text{is} \quad Q(t) = Q_0 \exp\left(-\frac{t}{RC}\right) = C V_0 \exp\left(-\frac{t}{\tau}\right)$$

Notice that at  $t = 0$ , the formula gives  $Q = Q_0$ .



In time  $\tau$ ,  $Q$  falls by a factor of  $\exp(-1) = 1/e \cong 0.37..$

In time  $2\tau$ ,  $Q$  falls by a factor of  $\exp(-2) = (1/e)(1/e) \cong 0.14..$

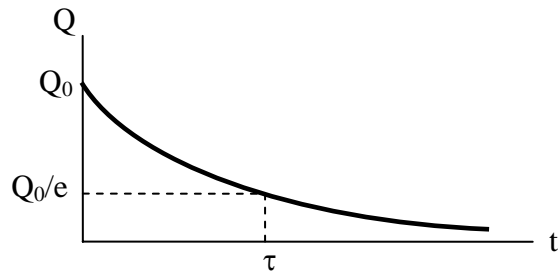
$\Rightarrow Q$  approaches zero asymptotically, and so does  $V$  and  $I$



$$Q(t) = Q_0 \exp\left(-\frac{t}{RC}\right) = Q_0 \exp\left(-\frac{t}{\tau}\right)$$

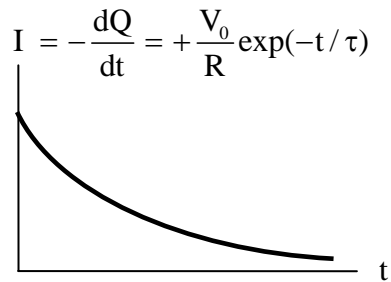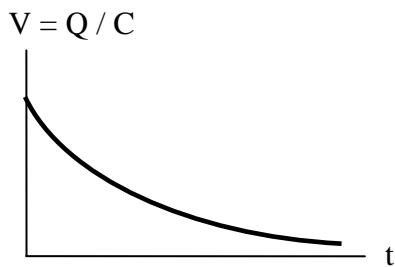

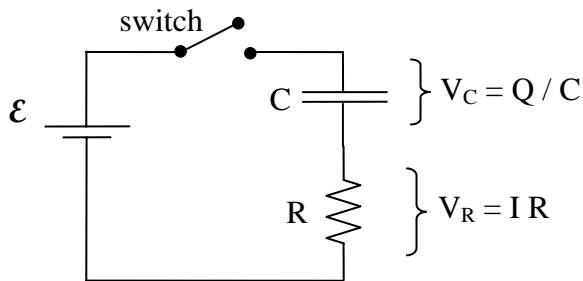**Example 2: More complex RC circuit:** Charging a capacitor with a battery.



Let's use symbol  $\mathcal{E}$  for battery voltage ( $\mathcal{E}$  short for emf) because there are so many other  $V$ 's in this example.

Before switch is closed,  $I = 0, Q = 0.$

Close switch at  $t = 0.$

Always true that  $\mathcal{E} = V_C + V_R$ , by Kirchoff's Voltage Law (Loop Law)

The charge  $Q$  on the capacitor and the voltage  $V_C = Q / C$  across the capacitor cannot change instantly, since it takes time for  $Q$  to build up, so ..

At  $t = 0+, Q = 0, V_C = 0, \mathcal{E} = V_C + V_R = V_R = I R \Rightarrow I_0 = \mathcal{E} / R$

Although  $Q$  on the capacitor cannot change instantly, the current  $I = dQ/dt$  can change instantly.

"Current through a capacitor" means  $dQ/dt$ . Even though there is no charge ever passing between the plates of the capacitor, there is a current going into one


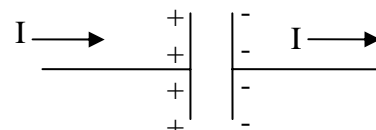


plate and the same current is coming out of the other plate, so it is as if there is a current passing through the capacitor.

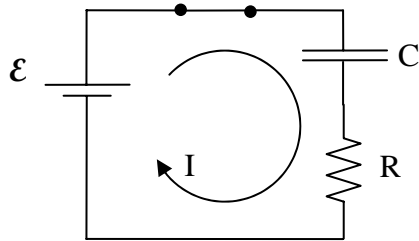


$$\mathcal{E} = V_R + V_C$$

$$\mathcal{E} = IR + \frac{Q}{C}, \quad I = +\frac{dQ}{dt}$$

$$\mathcal{E} = \frac{dQ}{dt}R + \frac{Q}{C}$$

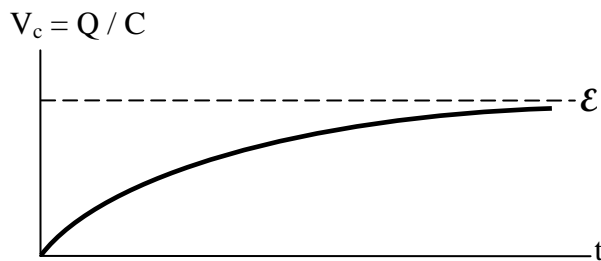Qualitatively, as  $t \uparrow$ ,  $Q \uparrow$ ,  $V_C = Q/C \uparrow$ ,  $V_R \downarrow$ ,  $I = V_R/R \downarrow$ . After a long time,  $t \gg \tau = RC$ , the current decreases to zero:  $I = 0$ ,  $V_C = \mathcal{E}$ ,  $Q = C \mathcal{E}$



Analytic solution:

$$V_C(t) = \mathcal{E}[1 - \exp(-t/RC)]$$

$$Q(t) = \mathcal{E} \cdot C [1 - \exp(-t/RC)]$$

Things to remember:

- Uncharged capacitor acts like a "short" ( a wire ) since  $V_C = Q / C = 0$ .
- After a long time, when the capacitor is fully charged, it acts like an "open-circuit" ( a break the wire). We must have  $I_C = 0$  eventually, otherwise  $Q \rightarrow \infty$ ,  $V_C \rightarrow \infty$ .