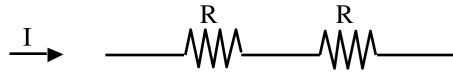


Two identical resistors are wired in series (one after the other).




If an electric current enters at the left, the current through the 2nd resistor is

- A: Equal to
- B: Half
- C: Smaller than, (but not necessarily $\frac{1}{2}$)
- the current through the first resistor.

©University of Colorado, Boulder (2008)

Your (slightly crazed) physics professor wants to grab both poles of a regular 12 V car battery. What happens?

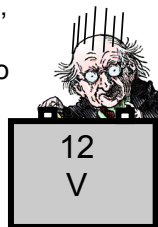
- A: STOP! Don't let him do it, certain death!
- B: Warning! (This is going to hurt a little.)
- C: Let him go for it. (He won't notice a thing...)
- D) I abstain from voting



©University of Colorado, Boulder (2008)

What if he says he's going to connect the poles with a screwdriver?

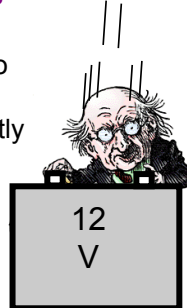- A: STOP! Don't let him do it, very bad idea!
- B: Warning! (This is slightly risky)
- C: Let him go for it.




©University of Colorado, Boulder (2008)

Two cylindrical resistors are made of the same material (same resistivity ρ).

Resistor 2 is twice as long and has twice the diameter of resistor 1. What is the ratio R_2/R_1 ?


- A) 2
- B) 4
- C) 1/2
- D) 1/4
- E) 1

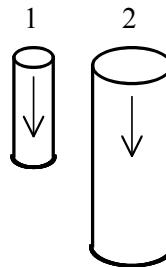

©University of Colorado, Boulder (2008)

A flashlight requires 2 AA (1.5V) batteries, and is arranged as shown. The bulb...

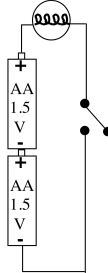
- A: has 1.5 V across it, & glows
- B: has 3 V across it, & glows
- C: has 3 V across it, & is dark
- D: has 0 V across it, & is dark
- E: has 0 V across it, & glows



©University of Colorado, Boulder (2008)

What about when I close the switch?
Now the bulb...

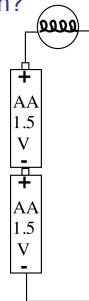- A: has 1.5 V across it, & glows
- B: has 3 V across it, & glows
- C: has 3 V across it, & is dark
- D: has 0 V across it, & is dark
- E: has 0 V across it, & glows



©University of Colorado, Boulder (2008)


First we had 1.5 V across that bulb,
later we put 3 V across the SAME
bulb. What happened to the POWER
dissipated by the bulb?

- A) Stayed the same
- B) Doubled
- C) Quadrupled
- D) Not sure/something else

©University of Colorado, Boulder (2008)

What if I reverse one battery?
Now the bulb...

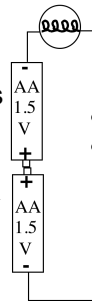- A: has 1.5 V across it, & glows
- B: has 3 V across it, & glows
- C: has 3 V across it, & is dark
- D: has 0 V across it, & is dark
- E: has 0 V across it, & glows



©University of Colorado, Boulder (2008)

Which bulb is brighter?

- A: A is brighter
- B: A is ON,
B is brighter
- C: A is OFF,
B is brighter
- D: Equal

