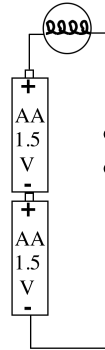


In the circuit shown, the bulb...


- A: has 1.5 V across it, & glows
- B: has 3 V across it, & glows
- C: has 3 V across it, & is dark
- D: has 0 V across it, & is dark
- E: has 0 V across it, & glows



©University of Colorado, Boulder (2008)

In the circuit shown, the bulb...

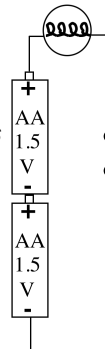- A: has 1.5 V across it, & glows
- B: has 3 V across it, & glows**
- C: has 3 V across it, & is dark
- D: has 0 V across it, & is dark
- E: has 0 V across it, & glows



©University of Colorado, Boulder (2008)

What if I reverse one battery?

Now the bulb...


A: has 1.5 V across it, & glows

B: has 3 V across it, & glows

C: has 3 V across it, & is dark

D: has 0 V across it, & is dark

E: has 0 V across it, & glows

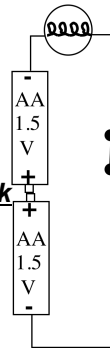


©University of Colorado, Boulder (2008)

Compare the power dissipated by a bulb (powered by one battery) if we swap out a 1.5 V and replace it with a 3 V battery. The power:

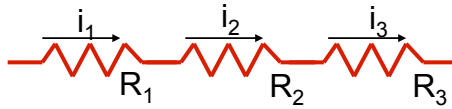- A) Stays the same
- B) Doubles
- C) Quadruples
- D) Something else!
- E) ??

©University of Colorado, Boulder (2008)

Take the case where
 $R_1 = 5 \Omega$, $R_2 = 10 \Omega$, and $R_3 = 20 \Omega$
If $i_1 = 5.0 \text{ A}$, what are the other currents?




- A) $i_2 = 10 \text{ A}$, $i_3 = 20 \text{ A}$
- B) $i_2 = 2.5 \text{ A}$, $i_3 = 1.25 \text{ A}$
- C) $i_2 = 1.25 \text{ A}$, $i_3 = 0.30 \text{ A}$
- D) $i_2 = 0.0 \text{ A}$, $i_3 = 0.0 \text{ A}$
- E) None of the above answers.

©University of Colorado, Boulder (2008)

What is the "equivalent resistance" of this circuit?

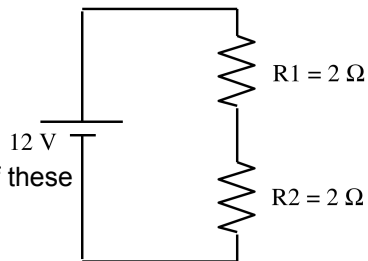
- A: 1Ω
- B: 2Ω
- C: 3Ω
- D: 4Ω
- E: None of these



©University of Colorado, Boulder (2008)

What is the current flowing through R2?

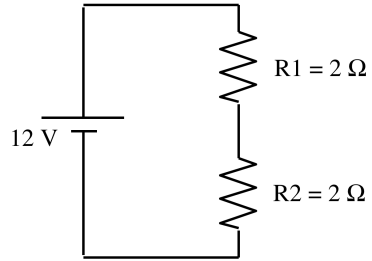
- A: 1.5 A
- B: 2 A
- C: 3 A
- D: 4 A
- E: 6 A



©University of Colorado, Boulder (2008)

What is the equivalent resistance for this circuit?

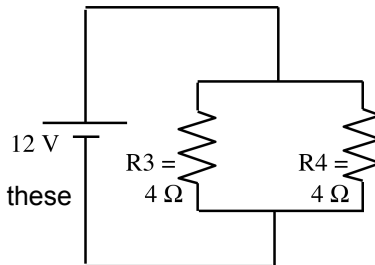
- A: $0.5\ \Omega$
- B: $2\ \Omega$
- C: $4\ \Omega$
- D: $8\ \Omega$
- E: None of these



©University of Colorado, Boulder (2008)

What is the current flowing through R3?

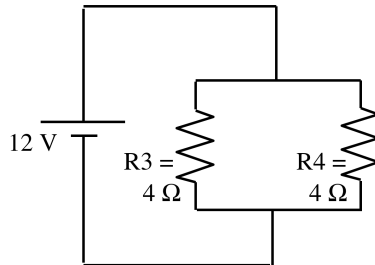- A: 1.5 A
- B: 2 A
- C: 3 A
- D: 4 A
- E: 6 A




©University of Colorado, Boulder (2008)

CT 29.12d'

What's the voltage drop across the 3Ω resistor, i.e. $\Delta V(AC)$?

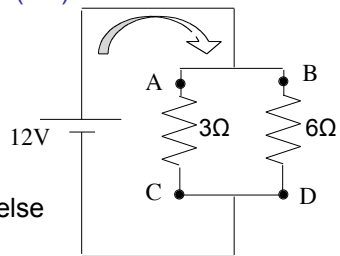
- A: 12 V
- B: 8 V
- C: 6 V
- D: 3 V
- E: something else



©University of Colorado, Boulder (2008)

A $1\ \Omega$ resistor is placed in parallel with a $10,000\ \Omega$ resistor as shown.

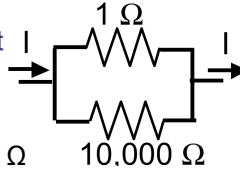The total, equivalent resistance of these two resistors in parallel is...



- A: a little less than $1\ \Omega$
- B: a little more than $1\ \Omega$.
- C: about $5000\ \Omega$
- D: a little less than $10,000\ \Omega$
- E: a little more than $10,000\ \Omega$


©University of Colorado, Boulder (2008)

AC: Alternating Current

©University of Colorado, Boulder (2008)

A 100 W (average power) light bulb is plugged into a normal (120 V RMS, 60 Hz, AC) socket. What is the *peak power* output to the bulb?

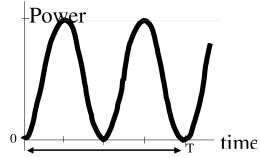- A) 50 W
- B) 100 W
- C) 200 W
- D) Something else
- E) ??



©University of Colorado, Boulder (2008)