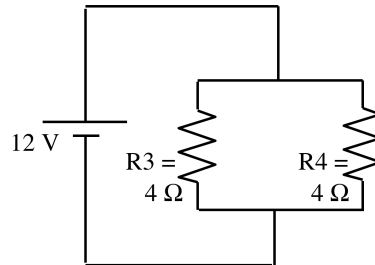


What is the current flowing through R3?

- A: 1.5 A
- B: 2 A
- C: 3 A
- D: 4 A
- E: 6 A




©University of Colorado, Boulder (2008)

CT 29.12d'

What's the voltage drop across the 3Ω resistor, i.e. $\Delta V(AC)$?

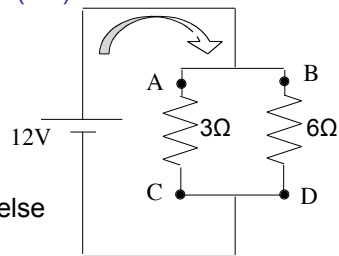
- A: 12 V
- B: 8 V
- C: 6 V
- D: 3 V
- E: something else



©University of Colorado, Boulder (2008)


This circuit has a fuse and a variable resistor R. If the resistance of R suddenly goes DOWN, is the fuse (or "circuit breaker")....

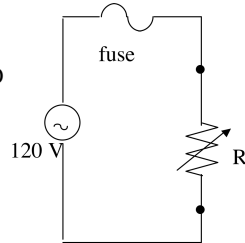- A: More likely to trip
- B: Less likely to trip



©University of Colorado, Boulder (2008)

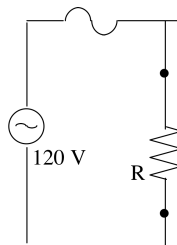If we start with a circuit with one resistor (R),




©University of Colorado, Boulder (2008)

If we start with a circuit with one resistor (R), and then add a second identical resistor (R) in *parallel*, is the fuse (or "circuit breaker")....

- A: more
- B: less
- C: equally

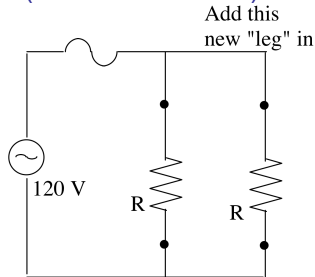...likely to trip (than before the new leg was added)




©University of Colorado, Boulder (2008)

We start with the left circuit with bulb (A).

If we add a second bulb (B) as shown on the right, what happens to bulb A?

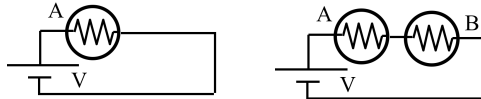- A) Bulb A is equally bright as it was before.
- B) Bulb A is dimmer than it was before
- C) Bulb A is brighter than it was before



©University of Colorado, Boulder (2008)

A household 40W light bulb and a 60W light bulb each has a filament with a certain resistance (when the bulb is on and hot).


How do the resistances of the filaments compare?

- A: $R_{40W} = R_{60W}$.
- B: $R_{40W} > R_{60W}$.
- C: $R_{40W} < R_{60W}$.
- D: Need more info.

©University of Colorado, Boulder (2008)

These two bulbs are now put in *series*. (which is not a normal thing to do) Which bulb glows brighter?

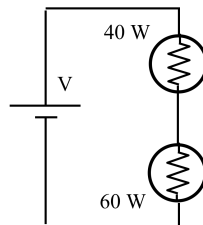- A: both have same brightness
- B: 40W is brighter
- C: 60W is brighter
- D: Not enough info




Hints: More power = brighter.
When light bulbs are *in series*, they have the same current.
Light bulbs are intended to operate at 120V.

©University of Colorado, Boulder (2008)

$R_1=10\ \Omega$, $R_2=5\ \Omega$. What's the voltage drop across the $10\ \Omega$, i.e. $\Delta V(AB)$?

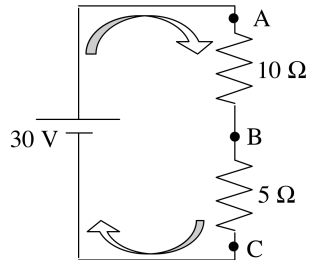- A: 30 V
- B: 20 V
- C: 15 V
- D: 10 V
- E: 0 V



©University of Colorado, Boulder (2008)