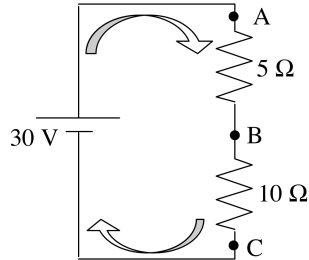


$R_1=5\ \Omega$, $R_2=10\ \Omega$. What's the voltage drop across the $10\ \Omega$ resistor, i.e. $\Delta V(BC)$?

- A: 30 V
- B: 20 V
- C: 15 V
- D: 10 V
- E: 0 V





©University of Colorado, Boulder (2008)

We start with the left circuit with bulb (A).

If we add a second bulb (B) as shown on the right, what happens to bulb A?

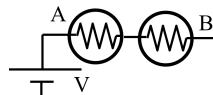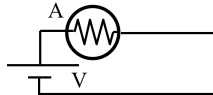- A) Bulb A is equally bright as it was before.
- B) Bulb A is dimmer than it was before
- C) Bulb A is brighter than it was before



©University of Colorado, Boulder (2008)

A household 40W light bulb and a 60W light bulb each has a filament with a certain resistance (when the bulb is on and hot).


How do the resistances of the filaments compare?

- A: $R_{40W} = R_{60W}$.
- B: $R_{40W} > R_{60W}$
- C: $R_{40W} < R_{60W}$
- D: Need more info.

©University of Colorado, Boulder (2008)

These two bulbs are now put in *series*. (which is not a normal thing to do) Which bulb glows brighter?

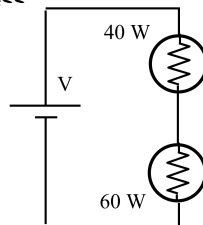- A: both have same brightness
- B: "40W" is brighter
- C: "60W" is brighter
- D: Not enough info




Hints: More power = brighter.
When light bulbs are *in series*, they have the same current.
Light bulbs are intended to operate at 120V.

©University of Colorado, Boulder (2008)

$R_1=10\ \Omega$, $R_2=5\ \Omega$. What's the voltage drop across the $10\ \Omega$, i.e. $\Delta V(AB)$?

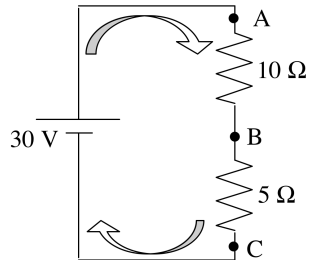
- A: 30 V
- B: 20 V
- C: 15 V
- D: 10 V
- E: 0 V



©University of Colorado, Boulder (2008)

What is $R(\text{equivalent})$, if each bulb has $R=10\ \Omega$

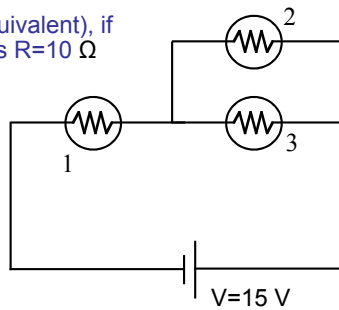
- A) 30 Ω
- B) 20 Ω
- C) 15 Ω
- D) 10 Ω
- E) Other/??



©University of Colorado, Boulder (2008)

A $1\ \Omega$ resistor is placed in parallel with a $10,000\ \Omega$ resistor as shown.

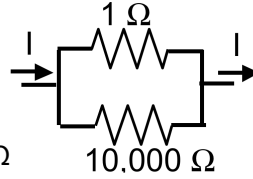The total, equivalent resistance of these two resistors in parallel is...



- A: a little less than $1\ \Omega$
- B: a little more than $1\ \Omega$.
- C: about $5000\ \Omega$
- D: a little less than $10,000\ \Omega$
- E: a little more than $10,000\ \Omega$

©University of Colorado, Boulder (2008)

Power=energy/time

So, energy = power*time

$1\ \text{J} = 1\ \text{W} * 1\ \text{second}$

$= 1\ \text{W s}$

©University of Colorado, Boulder (2008)

1 kW hr costs about \$0.10 in Colorado.
If you leave a 100 W bulb on all day (24 hours), **about how much did that cost?**

- A) Completely negligible, not even 1 cent!
- B) couple of cents
- C) about a quarter
- D) couple of bucks
- E) None of these is even close

©University of Colorado, Boulder (2008)