




# 3320 RLC-1




Having studied INDUCTANCE, let's consider how we might deal with R, L, & C in real-life circuits.

<u>Symbol</u>	<u>Circuit Relation</u>	<u>Geometry</u>	<u>Field</u>
	$Q = C V$ or, $I = C dV/dt$	$C = \epsilon_0 A/d$ (Parallel plates)	$E = \sigma_b / \epsilon_0$ Differen <sup>t</sup> $\sigma$ 's! $J = \sigma E$
	$V = I R$	$R = \rho L/A$ (uniform rod)	
	$V = -L \frac{dI}{dt}$	$L = \mu_0 n A \times N_{\text{turns}}$ (Long solenoid)	$B = \mu_0 n I$ or $\Phi_B = L I$

Kirchoff's Laws say  $\sum_{\text{around any closed loop}} \Delta V = 0$  and  $\sum_{\text{all currents entering any point (node) in a circuit}} I_{\text{in}} = 0$ .

"Solving a circuit" means, generally, finding  $I(t)$  through, +/or  $\Delta V(t)$  across, all circuit elements

### 3320 RLC-2

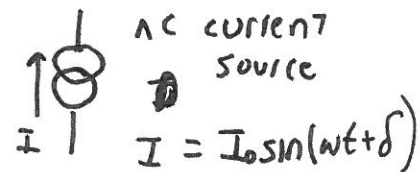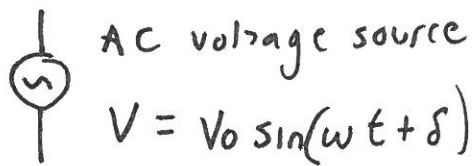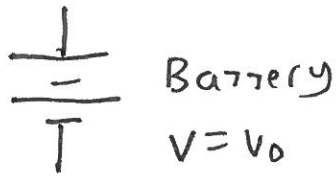

Notes:  $\epsilon_0 = 8.85 \cdot 10^{-12} \frac{\text{farad}}{\text{m}} \Rightarrow$  real life c's range from  
 $\underbrace{< 1 \text{ pf}}_{10^{-12} \text{ f}}$  to  $\underbrace{> 1 \text{ f}}$   
 needs serious dielectrics!


- Typical resistors range from  $< 1 \Omega$  to several  $\text{M}\Omega$

$\rightarrow \mu_0 = 4\pi \cdot 10^{-7} \frac{\text{H}}{\text{m}}$  (and  $L = \mu_0 \frac{N^2}{l} A$ ) means  
 real life  $L$  ranges typically from  
 $< 10^{-6} \text{ H} \rightarrow \sim 1 \text{ Henry}$ .

(Although inductors  $\Rightarrow \frac{dB}{dt} \neq 0 \Rightarrow$  might be worried that "voltage" doesn't mean anything, in fact it's generally OK. outside the inductor,  $B \approx 0$ , + usually it's well defined to talk about  $\Delta V$  for paths outside the inductor - but use "EMF" when needed!)

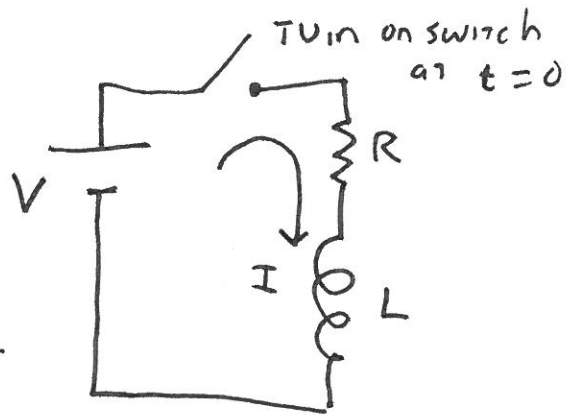Example: A simple RL circuit

$R$  might be distributed (in wires, battery, the inductor, etc). So might the inductance.



This is a model, + lets us see the general solution method.

(Intuitively,  $L$  doesn't "like" instant changes in current. So, we expect that at  $t=0$ , " $I$ " slowly changes from 0... after a long time (Steady state!) there are no more changes in anything,  $\Rightarrow \Delta V_{\text{inductor}} = 0$ ,  ~~$L$~~   <sup>$L$  acts</sup> like an ideal wire, + this is a simple (one  $R$ ) circuit.)

Kirchhoff says 
$$V - IR - L \frac{dI}{dt} = 0$$

I assume  $V$ ,  $R$ , &  $L$  are known, + we want  $I(t)$ .

$$L \frac{dI}{dt} + IR = V$$
 is a 1<sup>st</sup> order, inhomogeneous ODE.

There are several methods to solve this, I'll show two.

The first is direct, maybe familiar from Phys 2210. It gets unwieldy when there are lots of circuit elements.

The second is tricky, ("Phasors") + very powerful. We'll come back in a few pages + learn this method!

# 3320 RLC-4 -

## Sol'n Method #1

- 1) Find the general homogeneous sol'n to  $L \frac{dI_H}{dt} + I_H R = 0$  ↑
- 2) Find some particular sol'n of the full (inhomog) eq'n
- 3) Add these, to get a full general sol'n
- 4) Figure out the (one) arbitrary constant in  $I_H$  using initial conditions.

This method works for  $V = V_0$  (DC battery)

Also if  $V = V_0 \cos \omega t$  (AC power supply)

and thus, by superposition, we can in fact solve for any periodic  $V(t)$  (!!) because Fourier says (any periodic)  $V(t) = \sum_n V_n \cos \omega_n t$

So our method will be pretty general!

Here, the homogeneous eq'n  $\frac{dI_H}{dt} = -\frac{R}{L} I_H$

separates,  $\frac{dI}{I} = -\frac{R}{L} dt \Rightarrow I_H(t) = I_H(t=0) e^{-Rt/L}$

↑  
an as-yet arbitrary,  
undetermined constant.

(As <sup>might be</sup> ~~was~~ expected, over time, the resistor will kill off any starting current over time, but the inductor "stretches out" that time a bit.)

# 3320 RLC-5-

For particular sol'ns, you don't need generality. "Guess & check" is a perfectly acceptable method!

So e.g. if  $V = V_0 = \text{constant}$ ,  $L \frac{dI_p}{dt} + I_p R = V_0 = \text{constant}$

you might guess perhaps  $I_p(t) = a e^{-Rt/L} + b$  (? Maybe?)

Let's see! If so,  $\frac{dI_p}{dt} = -\frac{R}{L} a e^{-Rt/L}$ , + our ODE says

$$L \left( -\frac{R}{L} a e^{-Rt/L} \right) + (a e^{-Rt/L} + b) R = V_0$$

Hey, these cancel

leaving  $bR = V_0$ . Nice. It works, as long as  $b = V_0/R$


Recombining with  $I_H$  now (+ calling  $I_H(t=0) + a \equiv c$ )  
two unknowns

$$I(t) = I_p + I_H = c e^{-Rt/L} + V_0/R$$

$c$  is our one undetermined constant: find it from initial condition,  $I(0) = 0$

so  $c = -V_0/R$ , and (for our particular problem)

$$I(t) = \frac{V_0}{R} (1 - e^{-Rt/L})$$

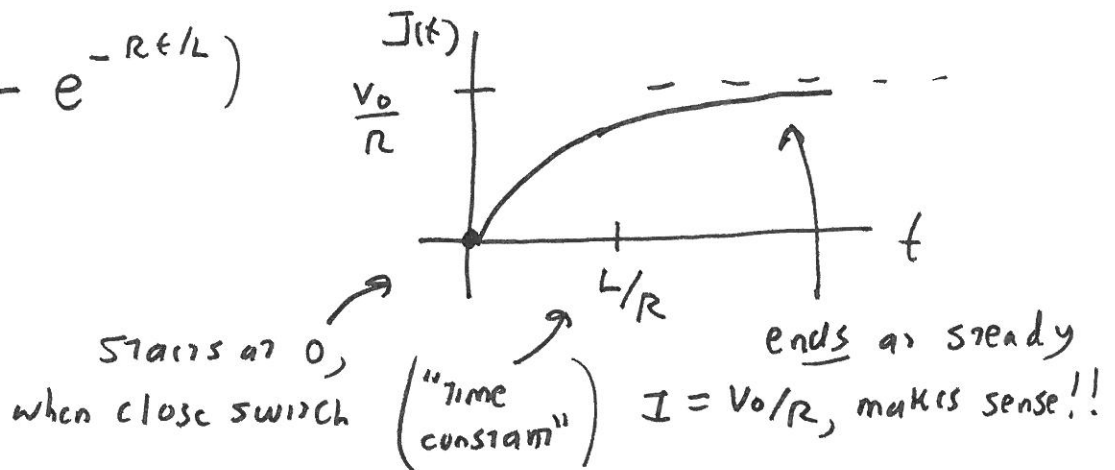

## 3320 RLC-6-

It's more interesting with AC voltage supplies (that's what one usually has available!). So, let's solve this circuit for

$$V = V_0 \cos(\omega t).$$

we have  $I_H$  already, just need a good guess for  $I_P(t)$ .

Well, sinusoidal driver might just result in sinusoidal current, so

$$\text{how about trying } I_P(t) = a \cos(\omega t + \phi)$$

not sure what these are, let's see!

It's a guess, we try it! If it works, great!

$$\text{so } L \frac{dI_P}{dt} + I_P R = V_0 \cos \omega t \quad \text{now.}$$

$$\text{plugging in our guess: } -L a \omega \sin(\omega t + \phi) + a R \cos(\omega t + \phi) = V_0 \cos \omega t$$

$$\text{using standard trig identities, } \begin{cases} \sin(a+b) = \sin a \overset{\text{typo!}}{\cos b} + \cos a \overset{\text{typo!}}{\sin b} \\ \cos(a+b) = \cos a \cos b - \sin a \sin b \end{cases}$$

we get

$$\begin{array}{rcl} -L a \omega \sin \omega t \cos \phi & - a R \sin \omega t \sin \phi & = 0 + \\ -L a \omega \cos \omega t \sin \phi & + a R \cos \omega t \cos \phi & = V_0 \cos \omega t \end{array}$$

ooh! we can make this work, for all times, if we set  
coeff of  $\sin \omega t$  on LHS = 0, + coeff of  $\cos \omega t = V_0$ ,

$$\text{i.e. } \begin{array}{l} \underline{\text{if}} \quad -L a \omega \cos \phi - a R \sin \phi = 0 \\ \underline{\text{and}} \quad -L a \omega \sin \phi + a R \cos \phi = V_0 \end{array} \left. \vphantom{\begin{array}{l} \underline{\text{if}} \\ \underline{\text{and}} \end{array}} \right\} \begin{array}{l} \text{Two eq'ns for} \\ \text{two unknowns,} \\ \text{a and } \phi! \end{array}$$

3320 RLC-7 -

The 1<sup>st</sup> eq'n says  $-L\omega \cos \phi = a R \sin \phi$

• would be true if  $a=0$ ... but that makes  $I_p=0$ , which is not useful to us.


• Or, it would be true if  $\tan \phi = -\frac{L\omega}{R}$ . Aha! This is it,

if  $\phi = \tan^{-1}\left(-\frac{L\omega}{R}\right)$ , then our  $I_p$  eq'n is satisfied.

thus  $\phi$  is not arbitrary, (+ is not "initial conditions"! it's fixed by the circuit + driver constants.

The 2<sup>nd</sup> eq'n was  $a(-L\omega \sin \phi + R \cos \phi) = V_0$ .

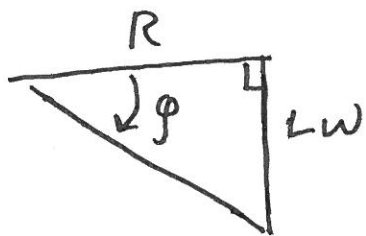The trick here is to draw a triangle showing  $\tan \phi = -\frac{L\omega}{R}$



From which I can just read off

$$\sin \phi = \frac{-L\omega}{\sqrt{R^2 + L^2\omega^2}} \quad \text{and} \quad \cos \phi = \frac{+R}{\sqrt{R^2 + L^2\omega^2}}$$

Putting that back in the 2<sup>nd</sup> eq'n will determine  $a$  for us:

$$a \cdot \left( \frac{+L^2\omega^2}{\sqrt{R^2 + L^2\omega^2}} + \frac{R^2}{\sqrt{R^2 + L^2\omega^2}} \right) = V_0, \quad \text{or} \quad a = \frac{V_0}{\sqrt{L^2\omega^2 + R^2}}$$

we did it. we found  $I_p = a \cos(\omega t + \phi)$

Both of these are in boxes on this page

Thus, our full sol'n is

$$I(t) = I_p + I_H = a \cos(\omega t + \phi) + I_{H0} e^{-Rt/L}$$

= persistent oscillatory response + Dying away piece.

Remember,  $a$  and  $\phi$  are determined on prev page

$I_{H0}$  is not, we can pick it still, to ~~we~~ satisfy initial condition  
 So e.g. if we closed the switch at  $t=0$ , so  $I(0)=0$ , then

$$I(t > 0) = a \cos(\omega t + \phi) - \underbrace{a \cos \phi}_{\text{chosen to make } I(0)=0!} e^{-Rt/L}$$

with amplitude  $a = \frac{V_0}{\sqrt{R^2 + L^2 \omega^2}}$  and phase shift  $\phi = \tan^{-1} \left( \frac{-L\omega}{R} \right)$

• If  $R$  is large,  $a$  is small. Makes sense, big  $R$  kills off long term currents.

• If  $\omega = 0$  (battery!)  $a \rightarrow V_0/R$  and  $\phi \rightarrow \tan^{-1} 0 = 0$   
 We knew that already, for DC voltage, long times  $\Rightarrow I = V_0/R$ ,  
 the inductor acts like an ideal wire when transients have died.

• If  $\omega \rightarrow \infty$ ,  $a \rightarrow 0$ . Inductors don't like rapid changes of  $\vec{I}$ ,  
 they suppress  $\uparrow$  "response" at high frequencies!

(Summary: This method works fine! But with more R's, C's, or L's, series + parallel, this could rapidly get too painful....)



Method #2, "Phasors". This is a tricky method to solve the same problem. It turns out to be very powerful + very common. The trick converts all that nasty, painful sin & cos trig stuff to the simple algebra of exponentials! It uses

Euler's theorem:  $e^{i\theta} = \cos \theta + i \sin \theta$ , or

$$\underline{e^{i\omega t} = \cos \omega t + i \sin \omega t}$$

So exponentials really "contain" all the math of sin's + cos's, but so much simpler! E.g.  $\frac{d}{dt} \cos \omega t = -\omega \sin \omega t$  is a new, linearly independent function.

But,  $\frac{d}{dt} e^{i\omega t} = i\omega e^{i\omega t}$ , just proportional. This saves a lot of grief.

So here's the trick. Instead of driving the circuit with  $v = V_0 \cos \omega t$ , let's pretend we drive the circuit with  $V_0 e^{i\omega t}$

A complex voltage? Well, in the end, we'll say

$$V_{\text{true}} = \text{Re}(V_{\text{fictitious}}), \text{ and } I_{\text{true}} = \text{Re}(I_{\text{fictitious}})$$

we can do this because the ODE is linear, so  $\text{Re}(I)$  arises

from  $\text{Re}(V)$ . Benefit: ODE becomes a (simple!) algebra problem

Cost: The sol'n looks complex, + we must remember to take the real part in the end!

Let's redo the same problem again with this method.

$$\text{So, } L \frac{dI}{dt} + IR = V(t) = \tilde{V} e^{i\omega t}$$

we have this (fictitious) driving voltage,  $\tilde{V} e^{i\omega t}$ . It's complex.

- Real (physical) voltage =  $\text{Re}(\tilde{V} e^{i\omega t})$

- If  $\tilde{V}$  is itself a complex constant, i.e. if  $\tilde{V} = V_0 e^{i\delta}$ ,

we can allow for drivers of the form  $V_0(\cos \omega t + \delta)$ , more general!

we once again really just need  $I_p$ . And again, we guess + check!

The guess here is guise simple, try  $I_p = \tilde{I} e^{i\omega t}$  (See what happens!)

$$L \frac{dI}{dt} + IR = \tilde{V} e^{i\omega t} \text{ is our ODE}$$

$$\text{Trial: } L \tilde{I} (i\omega) e^{i\omega t} + \tilde{I} R e^{i\omega t} = \tilde{V} e^{i\omega t}$$

Sweet! The  $e^{i\omega t}$  cancels out, and we have an algebra eq'n

$$L \tilde{I} i\omega + \tilde{I} R = \tilde{V}, \text{ or } \tilde{I} = \frac{\tilde{V}}{R + i\omega L}$$

That's really it.  $\tilde{I}$  is a constant, it's determined  $\uparrow$ , +

$$\left( \text{then } I_{\text{true}} = \text{Re}(I_{\text{fictitious}}) = \text{Re}(\tilde{I} e^{i\omega t}) + I_H \right)$$


$\hookrightarrow$  (From before)

We're done!

The sol'n looks like  $\vec{V} = \vec{I} \vec{R}$ , with  $\vec{R}$  now complex.

We call it the impedance or the complex impedance,  $\underline{Z}$ .

So Here

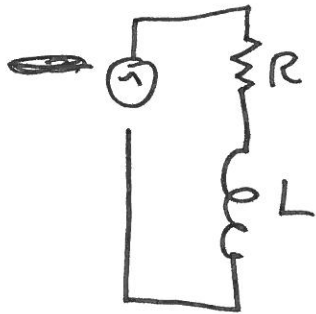

we get  $Z = R + i\omega L$

It's a simple series circuit, +  
the (complex) impedances just add.

This is a general rule! In any circuit, use

$Z_R = R$  impedance of resistor

$Z_L = i\omega L$  impedance of inductor


+ use your old "circuit simplification" tricks from Phys 2, like  
Z's in series add,  $1/Z$ 's in parallel add up to  $1/Z_{total}$  (etc)

(We'll come back to capacitors shortly, + prove

$Z_C = -\frac{i}{\omega C}$ , + then you can add them in too!)
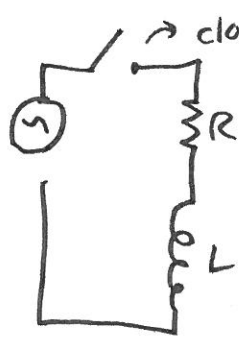
# RLC-12-

Let's return to our RL example and wrap it up:



we have  $\hat{V} = \hat{I} (R + i\omega L)$

and  $V_{\text{rve}} = \text{Re } \hat{V} e^{i\omega t}$


$I_{\text{rve}} = \text{Re } \hat{I} e^{i\omega t} = \text{Re } \frac{\hat{V} e^{i\omega t}}{R + i\omega L}$

In our original setup,  $V_{\text{real}} = V_0 \cos \omega t$ , so  $\hat{V} = V_0$ .

So for this case:  $I_{\text{rve}} = \text{Re} \left( \frac{V_0 e^{i\omega t}}{R + i\omega L} \right) \underset{\text{trick}}{=} \text{Re} \left( \frac{V_0 e^{i\omega t}}{R + i\omega L} \frac{R - i\omega L}{R - i\omega L} \right)$

so  $I = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \text{Re} \left( e^{i\omega t} (R - i\omega L) \right)$

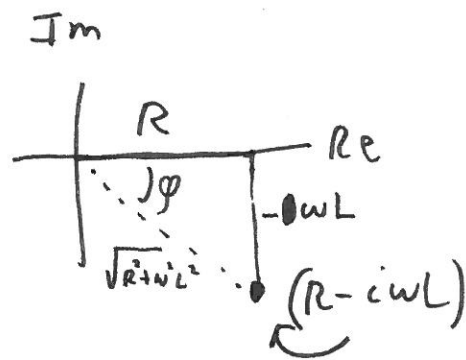Next standard trick: Write  $R - i\omega L$  in complex plane  $\rightarrow$



+ note that this point is simply

$\sqrt{R^2 + \omega^2 L^2} e^{i\phi}$  with, by inspection,  $\phi$  as shown =  $\tan^{-1} \frac{-\omega L}{R}$

So  $I = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \text{Re} (e^{i\omega t} \cdot e^{i\phi}) = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi)$

Exact same sol'n as we had before, (obtained just using  $V = IZ$ .)

Note: The method also works if  $V = V_0 \cos(\omega t + \delta)$ , just

use  $\hat{V} = V_0 e^{i\delta}$  (convince yourself!). Or, e.g. if  $V = V_0 \sin \omega t$ ,

just use  $\hat{V} = V_0 e^{-i\pi/2}$  (or, for that matter, take  $\text{Im}()$  instead of  $\text{Re}()$ )

## RLC -13-

What if the circuit has a capacitor?


$$\text{||} \quad V = \frac{Q}{C} \Rightarrow \frac{dV}{dt} = \frac{I}{C}, \text{ or } I = C \frac{dV}{dt}$$

so if  $V = \tilde{V} e^{i\omega t}$  then  $I = C \cdot i\omega \cdot \tilde{V} e^{i\omega t} = i\omega C V$


so this too looks like  $V = I "R"$ , but this time our

complex impedance is  $Z_c = \frac{1}{i\omega C}$  (Use "Z" instead of "R" whenever it's complex)


### Summary

$$Z = R$$


R

$$Z = i\omega L$$


L

$$Z = \frac{1}{i\omega C} = -\frac{i}{\omega C}$$


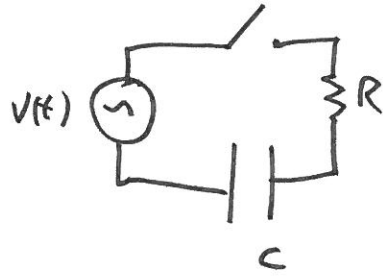
C

General procedure: Pretend you have a simple resistor circuit, using  $Z$  in place of  $R$ , and solve for  $V, I$  using usual phys 1120 (Kirchoff or "reducing equivalent resistors") methods.

That's it!

# RLC-14-

Example: An RC circuit



Turn it on @  $t=0$   
Suppose  $V = V_0 \cos \omega t$

Think of this as two "Z"s in series,

$$Z_{\text{tot}} = Z_R + Z_C = R - i/\omega C$$

then  $\hat{V} = \hat{I} Z \Rightarrow \hat{I} = \frac{\hat{V}}{R - i/\omega C}$  and  $I_{\text{real}} = V_0 \operatorname{Re} \frac{e^{i\omega t}}{R - i/\omega C}$

use usual trick,  $I = V_0 \operatorname{Re} \left( \frac{e^{i\omega t}}{R - i/\omega C} \frac{R + i/\omega C}{R + i/\omega C} \right) = \frac{V_0}{R^2 + \frac{1}{\omega^2 C^2}} \operatorname{Re} \left( e^{i\omega t} \frac{R + i/\omega C}{R + i/\omega C} \right)$

Draw a picture tells me  $e^{i\phi} = \frac{R}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} + \frac{i/\omega C}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$   
 $\phi = \tan^{-1} \frac{1}{\omega C R}$

so  $I = \frac{V_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \cos(\omega t + \phi)$ . That's it for  $I_{\text{particular}}$

Still need  $I_{\text{homog}}$ , from  $0 = IR + Q/C$  or  $\frac{dI}{dt} R = -\frac{I}{C}$

so  $\frac{dI}{I} = -\frac{1}{RC} dt \Rightarrow I_H = I_0 e^{-t/RC}$

so  $I_{\text{tot}} = \frac{V_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \cos(\omega t + \phi) + I_0 e^{-t/RC}$   
↑ transient, dies off  
to be determined  
↪ steady sol'n.

Init condition:  $\Delta V_{\text{capac}}$  cannot suddenly change! If it was 0 before,

then after  $t=0^+$ , we have  $V_0 = IR$ , or  $I(t=0) = V_0/R$


(I can jump instantly in this case!)

## RLC - 15 -

$$I = \frac{V_0}{\sqrt{R^2 + 1/\omega^2 C^2}} \cos(\omega t + \phi) + \underbrace{\left( \frac{V_0}{R} - \frac{V_0 \cos \phi}{\sqrt{R^2 + 1/\omega^2 C^2}} \right)}_{\text{Picked to make } I_0 = V_0/R} e^{-t/RC}$$

- Time constant is "RC"
- After several RC times, circuit oscillates @ driver frequency  $\omega$
- If  $\omega \rightarrow 0$ ,  $I_{\text{long term}} \rightarrow 0$ , the capacitor blocks steady current!
- If  $\omega \rightarrow \infty$ ,  $I_{\text{long term}} \rightarrow \frac{V_0}{R} \cos(\omega t)$ , like the capacitor isn't even there.

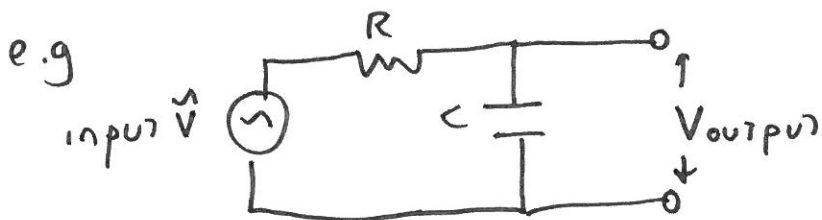Many people prefer to have an output voltage as their signal, so



We know  $I$  in this circuit,  
so  $V_{out} = I Z_C = I (-i/\omega C)$

$$\text{Thus } V_{out} = \frac{V_{in}}{R - \frac{i}{\omega C}} \cdot \frac{-i}{\omega C} = V_{in} \cdot \frac{1}{1 + i\omega RC}$$


If  $\omega \rightarrow 0$ ,  $V_{out} = V_{in}$ , the capac does'n't do anything

If  $\omega \rightarrow \infty$ ,  $V_{out} \rightarrow 0$ . This is a "low pass filter",

it suppresses high frequency parts of the signal.
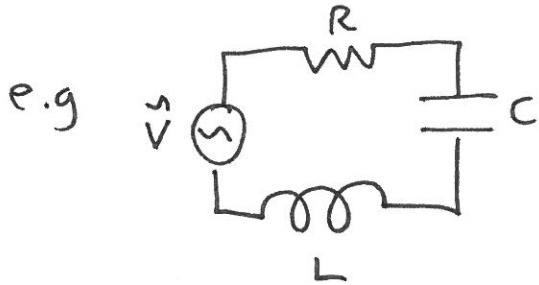
## RLC - 16 -

In general, any circuit like this is no harder than a phys 1120 circuit.



just use  $Z = R - \frac{i}{\omega C} + i\omega L$

and then  $\tilde{v} = \tilde{I} Z$

Parallel, series: just treat it like a simple resistor network.  
(The power of phasors!)