
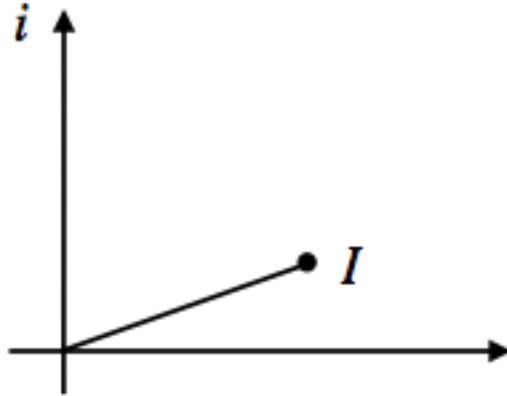


## Complex Impedence

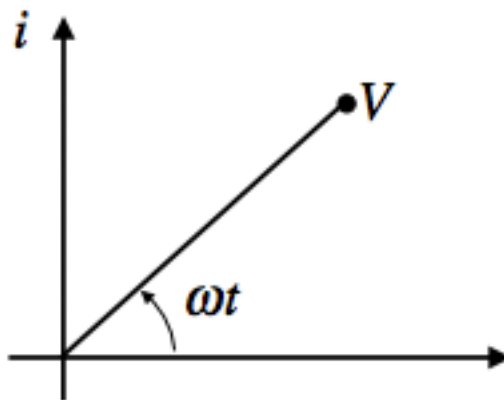A. Given  $Z = 2\exp(i\pi/4)$  and the complex number  $I$  shown in the diagram below, plot the complex number  $V = I \cdot Z$



Given  $V = V_0 \exp(i\omega t)$  and  $Z = 2\exp(-i\pi/2)$ , plot the complex number  $I = V/Z$  at the instant in time shown in the diagram below.



## Complex Impedance

**B.** For the same situation as before, with  $V = V_0 \exp(i\omega t)$  and  $Z = 2 \exp(-i\pi/2)$ , sketch the real (physical) values of  $V$  &  $I$  as functions of time in the graphs below.



Does the current *lead* or *lag* the voltage? Make sure your answers on this page are consistent with the phasor diagram you drew on the previous page for the same situation.


▽ You may continue, but be sure to check your answers to this part with an instructor.

## Complex Impedance

**C.** The complex impedances for the following circuit elements are:

$$Z_R = R \quad Z_L = i\omega L \quad Z_C = \frac{1}{i\omega C}$$

What is  $Z_{TOTAL}$  for this circuit?

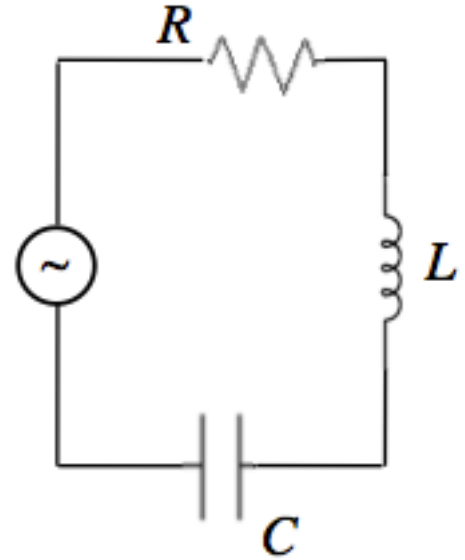

Write  $Z_{TOTAL}$  in the form  $a + ib$ .

**D.** For graphing purposes, assume that  $\omega L > 1/\omega C$ . Sketch  $Z_R$ ,  $Z_C$ ,  $Z_L$ , and show how they add as vectors to get  $Z_{TOTAL}$ .



Under what circumstances does the current *lead* the voltage?

Under what circumstances are the current and voltage *in phase*?